



Figure 1

This circuit exhibits a deadband for signals more positive than an arbitrary voltage, which R_1 determines.