



Figure 3 Dividing down the high-common-mode voltage introduces huge errors, even with precision components, making this approach impractical.