



Figure 2

Using the microcontroller's internal ADC, you need only two I/O pins to control 16 keys.