



Figure 1

This flyback topology produces negative output voltage from positive inputs.