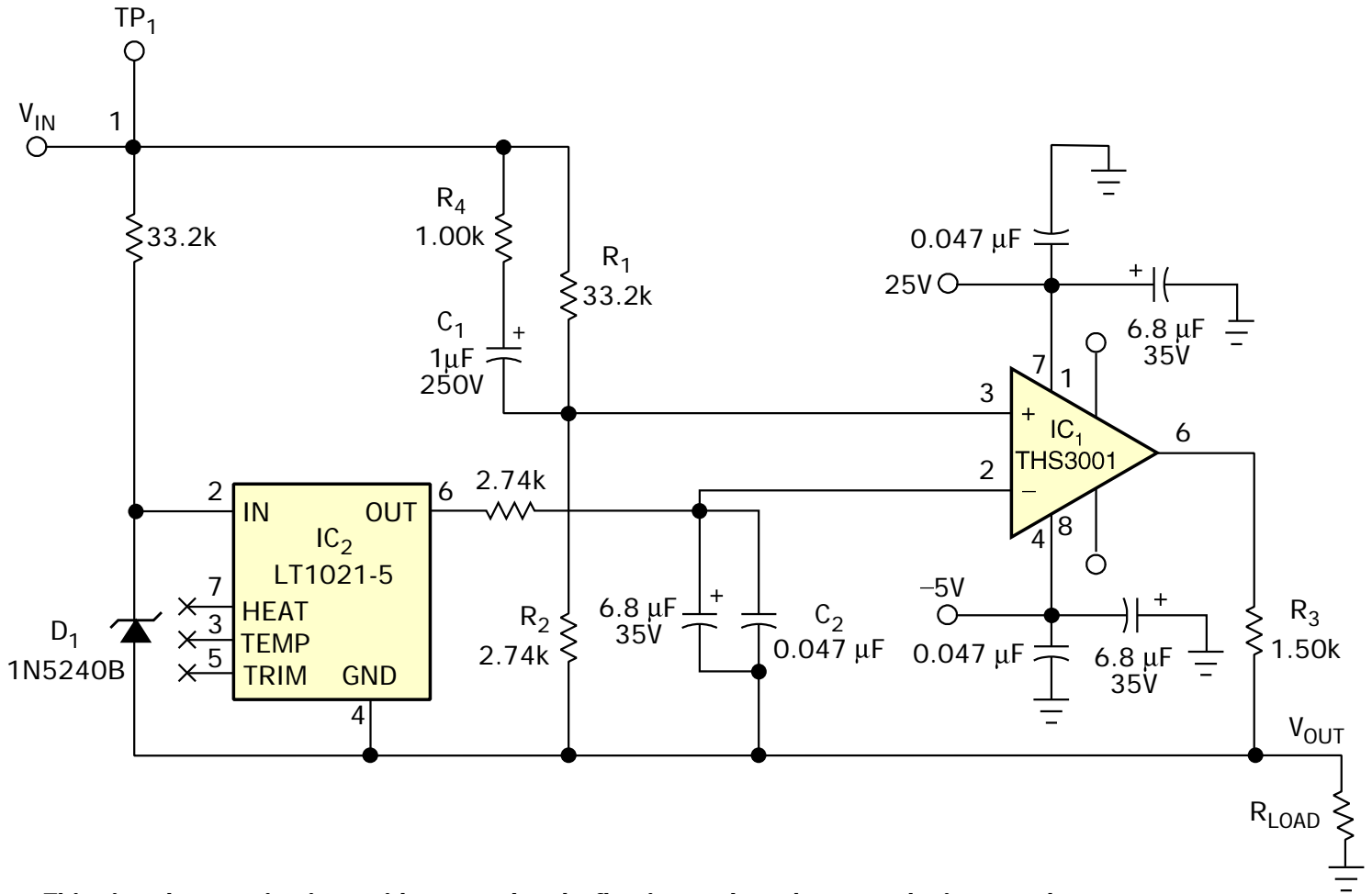


Figure 2



This virtual-zener circuit provides a regulated, "floating" voltage between the input and output.