



**Figure 2**

This VCO uses an OTA and a hysteretic comparator to deliver a reciprocal ( $1/x$ ) response to the control voltage.