



Figure 3

The output of the exclusive-OR circuit in Figure 2 is high only when the input frequency is between defined limits.