



Figure 1

A Class D audio amplifier, IC₁, helps implement this simple motor-speed controller.