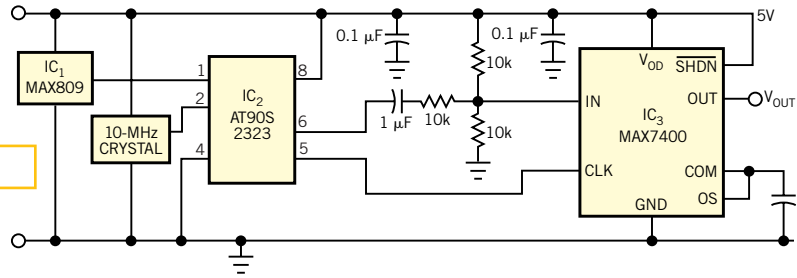


Figure 1



By removing harmonics from a square wave, this circuit generates an accurate and adjustable sine-wave output.