



**Figure 1**

This ideal 4- to 20-mA current transmitter has one voltage-controlled current source and one fixed current source.