



Figure 1

In this classic PWM-controller configuration, R_2 is the sensing resistor for the output current.