



**Figure 3**

Transistor  $Q_2$  suppresses (blanks) leading-edge spikes that could falsely trigger a PWM comparator.