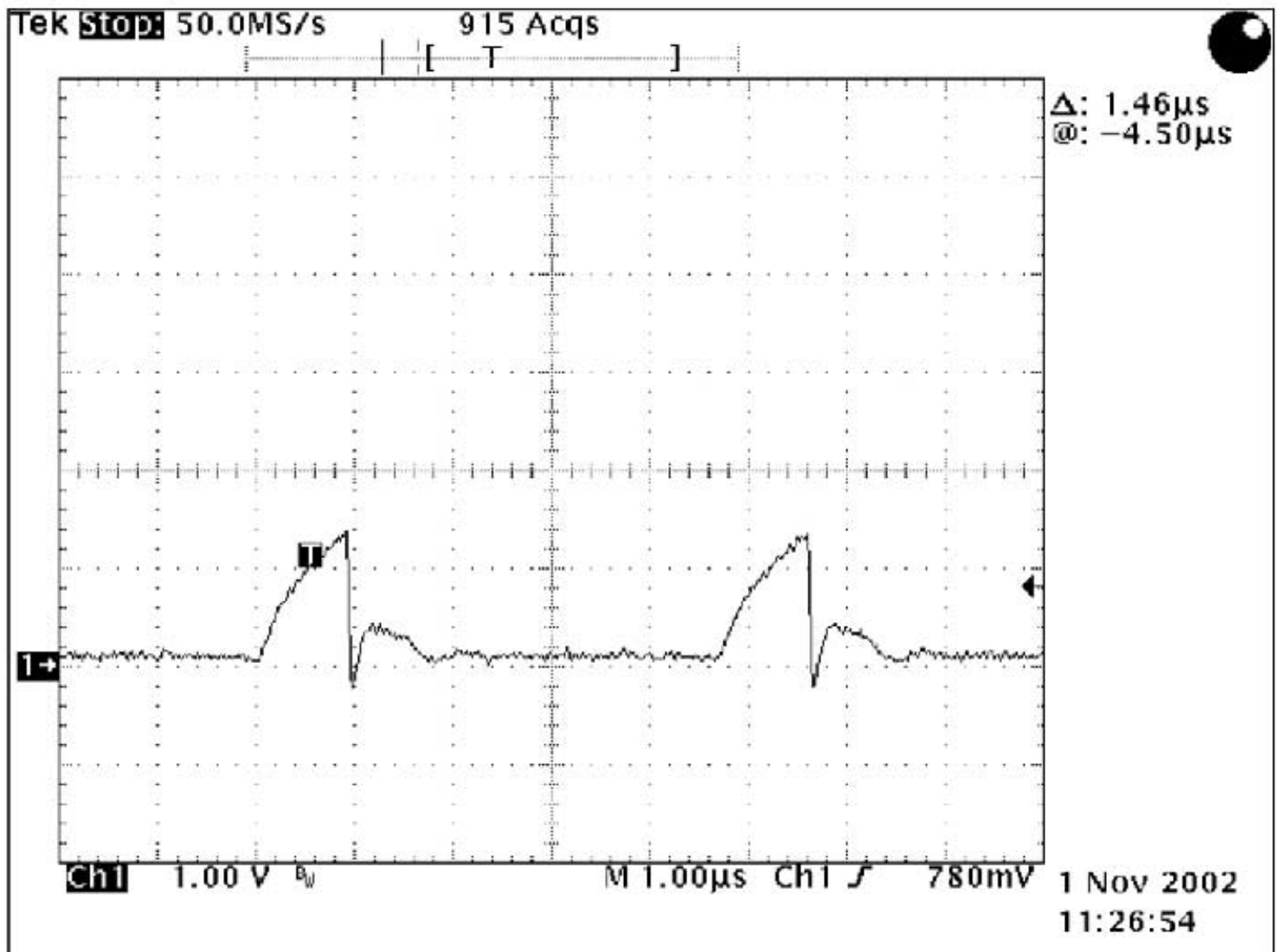


Figure 5



After adding the blanking circuit of Figure 3, the converter works normally.