



Figure 1

In this sine-wave oscillator, the output frequency is dependent only on the value of the grounded resistor R₁.