



**Figure 1**

**NOTE:**  
WHITE LED REQUIRES  $R_3$  AND  $D_2$ .

**This circuit delivers virtually constant luminosity for a white or a yellow LED.**