



Figure 1

This circuit does not use the shutdown pin of the PWM IC; instead, it relies on the error amplifier's output to provide current limit.