



Figure 1

(a)

(b)

You can incorporate hiccup circuitry (a) into your PWM-control scheme, using a typical shunt regulator (b) to regulate the supply voltage to the PWM chip.