



Figure 1

To free up a stuck I²C bus, this circuit controls the supply voltage to force a hardware reset.