



Figure 1

A 5V-powered, chopped bipolar amplifier (a) has noise of approximately 40 nV with 0.05 μV/°C drift in a 0.1- to 10-Hz bandwidth (b).

(a)