



Figure 3

A bandpass filter, driven by IC₁'s oscillation loop (a), continuously rings at resonance to produce cosine and sine outputs (b, traces B and C, respectively). A zener clamp (Trace A) sets the sine and cosine outputs' amplitude.