



Figure 7

A 1%-accurate interval generator has a dynamic range of 20×10^6 to 1 (a). The trigger-input pulse (b, Trace A) sets the circuit's Q output high (Trace B), and the LTC1799 oscillator (Trace C) clocks the counter until the counter output-biases the inverter low to reset the circuit output (Trace D).