



**Figure 1**

**This circuit is a universal level shifter for ac signals; it accommodates any interface standard.**