



**Figure 1**

It's easy to effect an interface of a 12-bit serial ADC to a PC.