



Figure 1 In a full synchronizer circuit, the signal-crossing clock domains should pass from the originating flip-flop in the original clock domain to the first flip-flop of the synchronizer without passing through any combinational logic between the originating flip-flop and the first flip-flop of the synchronizer.