



**Figure 2**

The edge-detecting synchronizer circuit adds a flip-flop to the output of the level synchronizer.