



**Figure 1**

In this equivalent circuit, you should maximize the coupling capacitances,  $C_1$  and  $C_2$ , and minimize the stray capacitances,  $C_3$ ,  $C_4$ , and  $C_5$ .