



This circuit produces waveforms of variable frequency and duty cycle. Further, the frequency and duty cycle are independent of each other.