



**Figure 1**

An active-feedback amplifier is ideal for current-sensing applications.