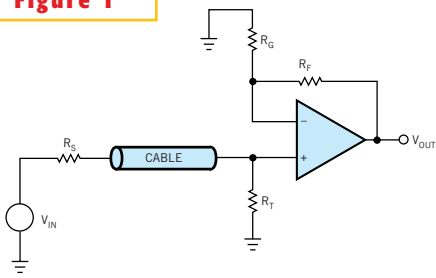


**Figure 1**



**A single-ended transmission line drives a noninverting op-amp receiver with no interaction with the op-amp resistances.**