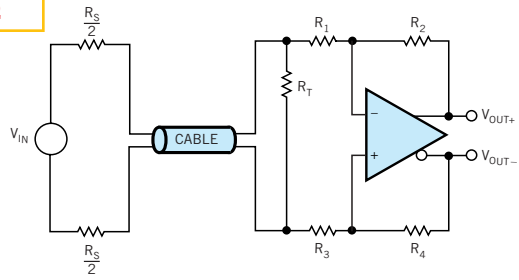


**Figure 2**



The fully-differential-termination scheme is much more complicated than the single-ended scheme because the calculations involve the gain-setting resistors.