



Figure 2

By varying one resistor, you can adjust the cutoff frequency over 20 Hz to 20 kHz.