



Figure 1

This circuit delivers a stable, precision dose of current to an LED.