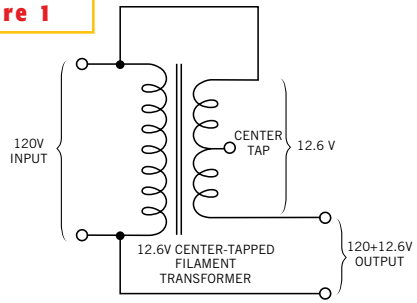


**Figure 1**



**You can use a small, inexpensive filament transformer to buck or boost the ac-line voltage.**