



NOTES: $A_{IC2} = 1 + \frac{50\text{ k}\Omega}{R_G}$
 IS THE GAIN FOR THE INA121P.
 IN THIS EXAMPLE, $R_G = \infty$, SO GAIN $A_{IC2} = 1$.

Figure 1 This current reference delivers an output that's a linear function of the input voltage.