



A variable delay triggers a pulse generator with a rise time of less than 1 nsec. The charge line at Q5's collector determines the output width: about 10 nsec. You can set the output pulse occurrence before, during, or after the trigger output.