



**Figure 4** The pulse generator's waveforms include the clock (Trace A), Q2's collector ramp (Trace B), the trigger output (Trace C), and the pulse output (Trace D). A delay sets the output pulse to occur about 170 nsec after the trigger output.