



Figure 1

This latching motor controller uses current sensing, rather than switches, to stop the motor.