



**Figure 1**

Fully differential termination is more complicated than the single-ended scheme, because you must take the gain-setting resistors into account when doing the calculations.