



**Figure 1**

A DDS circuit combines with a comparator and a microcontroller with an internal DAC and ADC to generate high-resolution PWM outputs.