



Figure 3

Applying different thresholds to the comparator in the circuit of Figure 1 has these effects.