



**Figure 1**

An xDSL driver uses current-feedback technology to make an efficient home-power-line driver.