



**Figure 1**

This 4 to 18V-input, 12V-output SEPIC has short-circuit protection.