



Figure 1

This circuit attenuates and level-shifts a $\pm 10V$ differential signal while operating from a single 5V supply.