



**Figure 2**

Capacitor  $C_2$  shunts  $C_{1A}/C_{1B}$  and reduces ac common-mode-rejection errors arising from component mismatch.