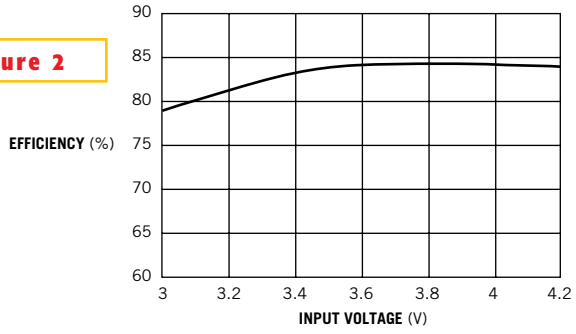


Figure 2



This curve shows the efficiency of the circuit in Figure 1 for 15-mA LED current and 3 to 4.2V battery voltage.