



Figure 1

This circuit is a programmable, temperature-compensated log-ratio amplifier.