



Figure 1

This soft-start circuit reduces inrush current, thereby prolonging lamp life.