



Figure 2

NOTE: SELECT R_1 AND R_4 TO SET THRESHOLD.

This variation on Figure 1's circuit can handle higher voltages.