



**Figure 1**

**This 5V supply, which you obtain by reducing the 3.3V input with a low-dropout regulator and doubling that output with a charge pump, minimizes the charge-pump output impedance by feeding 5V back to the regulator.**