



Figure 1

You can obtain four-quadrant power-supply operation by using a power op amp in the output section.